

BEE (Formulas)

Chapter 2

FORMULAS

2-1	$Q = \frac{\text{number of electrons}}{6.25 \times 10^{18} \text{ electrons/C}}$	Charge
2-2	$V = \frac{W}{Q}$	Voltage equals energy divided by charge.
2-3	$I = \frac{Q}{t}$	Current equals charge divided by time.
2-4	$G = \frac{1}{R}$	Conductance is the reciprocal of resistance.
2-5	$A = d^2$	Cross-sectional area equals the diameter squared.
2-6	$R = \frac{\rho l}{A}$	Resistance is resistivity times length divided by cross-sectional area.

Ch 3

FORMULAS

3-1	$I = \frac{V}{R}$	Form of Ohm's law for calculating current
3-2	$V = IR$	Form of Ohm's law for calculating voltage
3-3	$R = \frac{V}{I}$	Form of Ohm's law for calculating resistance

Ch 4

FORMULAS

4-1	$P = \frac{W}{t}$	Power equals energy divided by time.
4-2	$P = I^2 R$	Power equals current squared times resistance.
4-3	$P = VI$	Power equals voltage times current.
4-4	$P = \frac{V^2}{R}$	Power equals voltage squared divided by resistance.
4-5	$\text{Efficiency} = \frac{P_{\text{OUT}}}{P_{\text{IN}}}$	Power supply efficiency
4-6	$P_{\text{OUT}} = P_{\text{IN}} - P_{\text{LOSS}}$	Output power is input power less power loss.

Ch 5

FORMULAS

- 5-1 $R_T = R_1 + R_2 + R_3 + \cdots + R_n$ Total resistance of n resistors in series
- 5-2 $R_T = nR$ Total resistance of n equal-value resistors in series
- 5-3 $V_S = V_1 + V_2 + V_3 + \cdots + V_n$ Kirchhoff's voltage law
- 5-4 $V_S - V_1 - V_2 - V_3 - \cdots - V_n = 0$ Kirchhoff's voltage law stated another way
- 5-5 $V_x = \left(\frac{R_x}{R_T}\right)V_S$ Voltage-divider formula
- 5-6 $P_T = P_1 + P_2 + P_3 + \cdots + P_n$ Total power

Ch 6

FORMULAS

- 6-1 $I_{IN(1)} + I_{IN(2)} + \cdots + I_{IN(n)} = I_{OUT(1)} + I_{OUT(2)} + \cdots + I_{OUT(m)}$ Kirchhoff's current law
- 6-2 $R_T = \frac{1}{\left(\frac{1}{R_1}\right) + \left(\frac{1}{R_2}\right) + \left(\frac{1}{R_3}\right) + \cdots + \left(\frac{1}{R_n}\right)}$ Total parallel resistance
- 6-3 $R_T = \frac{R_1 R_2}{R_1 + R_2}$ Special case for two resistors in parallel
- 6-4 $R_T = \frac{R}{n}$ Special case for n equal-value resistors in parallel
- 6-5 $R_x = \frac{R_A R_T}{R_A - R_T}$ Unknown parallel resistor
- 6-6 $I_x = \left(\frac{R_T}{R_x}\right)I_T$ General current-divider formula
- 6-7 $I_1 = \left(\frac{R_2}{R_1 + R_2}\right)I_T$ Two-branch current-divider formula
- 6-8 $I_2 = \left(\frac{R_1}{R_1 + R_2}\right)I_T$ Two-branch current-divider formula
- 6-9 $P_T = P_1 + P_2 + P_3 + \cdots + P_n$ Total power
- 6-10 $R_{open} = \frac{1}{G_{T(calc)} - G_{T(meas)}}$ Open branch resistance

Ch 7

FORMULAS

- 7-1 $I_{BLEEDER} = I_T - I_{RL1} - I_{RL2}$ Bleeder current
- 7-2 $R_X = R_V \left(\frac{R_2}{R_4}\right)$ Unknown resistance in a Wheatstone bridge
- 7-3 $\Delta V_{OUT} = \Delta R_{therm} \left(\frac{V_S}{4R}\right)$ Thermistor bridge output

Ch 8

FORMULAS

Δ -to-Y Conversions

$$8-1 \quad R_1 = \frac{R_A R_C}{R_A + R_B + R_C}$$

$$8-2 \quad R_2 = \frac{R_B R_C}{R_A + R_B + R_C}$$

$$8-3 \quad R_3 = \frac{R_A R_B}{R_A + R_B + R_C}$$

Y-to- Δ Conversions

$$8-4 \quad R_A = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$$

$$8-5 \quad R_B = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$$

$$8-6 \quad R_C = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$$