

MILITARY COLLEGE OF SIGNALS  
BESE 16 (A@B) COURSE  
Mid Term Exam

Subj: BEE

Instr: Muhammad Saleem®


Marks: 30

Time: 1-1/2 Hrs

Note: - Attempt all questions, Make neat and clean diagram where required.


Question-1

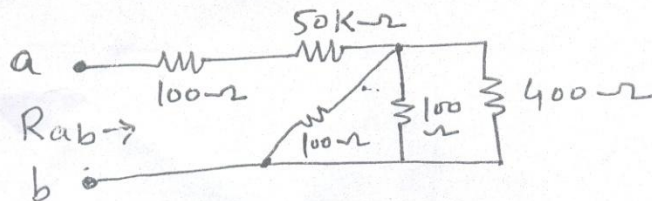- a. Find charge entering the terminal between  $t = 1$  second and  $t = 3$  second, if current is  $(3t^2 - t)$  A. (6)
- b. using source transformation Technique convert ideal 24 V DC source to equivalent current source. (2)
- c. Find  $R_{ab}$  in the circuit (2)



Question No-2 :-

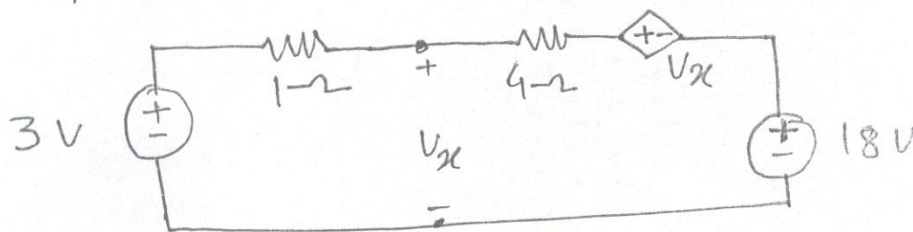
- a. Compute charge on 8 million proton and 4000 electrons. (2)
- b. Compute  $V_x$  in the given circuit (3)




- c. Total charge entering the terminal is  $Q = 6t \sin 4\pi t$  mc calculate current at time  $t = 0.5$  second. (3)
- d. Differentiate between voltage and emf, and potentiometer and rheostat. (2)

QUESTION NO - 3

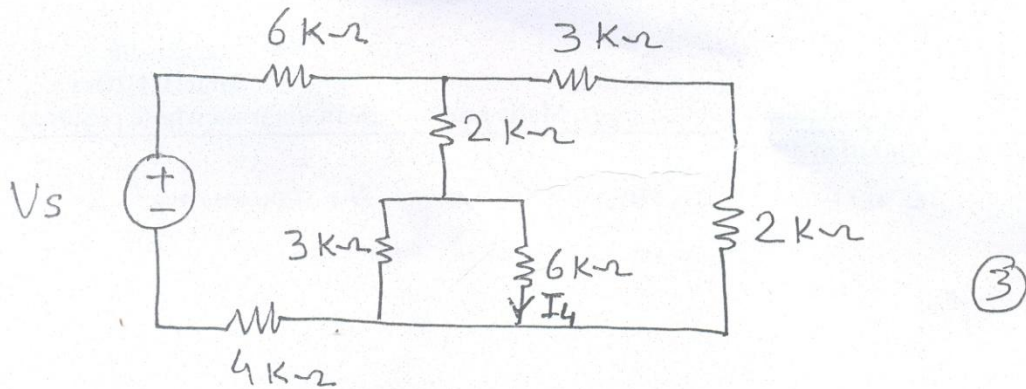
a. Find  $V_s$  if  $I_4$  is  $\frac{1}{2}$  mA



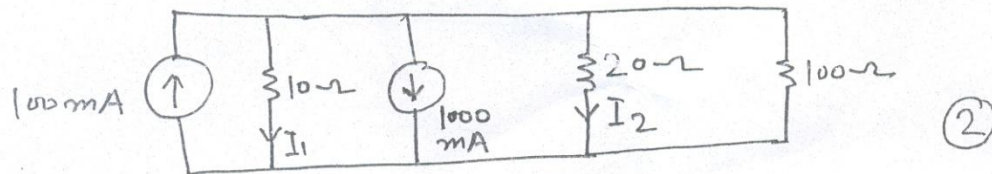b. Find  $I_1$  and  $I_2$  using current division formula.



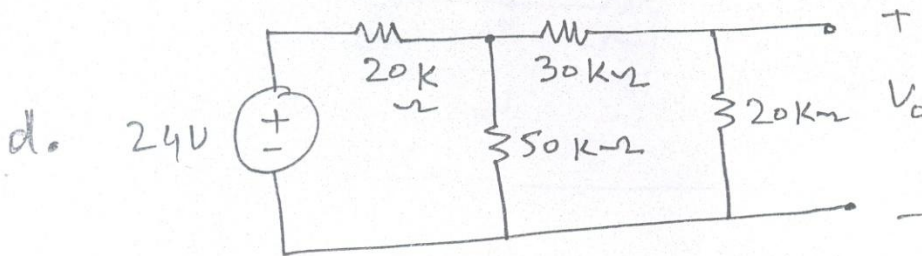c. Define electric shock, linear Resistance, branch, Node and Dependent source. (2.5)



compute  $V_o$  using any technique.

(2.5)

( Good Luck )

MILITARY COLLEGE OF SIGNALS  
BESE 16 (A@B) COURSE  
Mid Term Exam

Subj: BEE

Marks: 30

Instr: Muhammad Saleem®

Time: 1-1/2 Hrs

Note: Attempt all questions, Make neat and clean diagram where required.

Question-1

a-  $i = (3t^2 - t) \text{ A}$

$$q = \int_{t=1}^{t=3} i \, dt$$

$$q = \int_1^3 (3t^2 - t) \, dt$$

$$q = \left[ \frac{3t^3}{3} - \frac{t^2}{2} \right]_1^3 = \left[ t^3 - \frac{t^2}{2} \right]_1^3$$


$$= \left[ (3)^3 - \frac{(3)^2}{2} \right] - \left[ (1)^3 - \frac{(1)^2}{2} \right]$$

$$[27 - 4.5] - [1 - \frac{1}{2}]$$

$$(22.5) - \frac{1}{2} = 22 \text{ C}$$

$q = 22 \text{ C}$

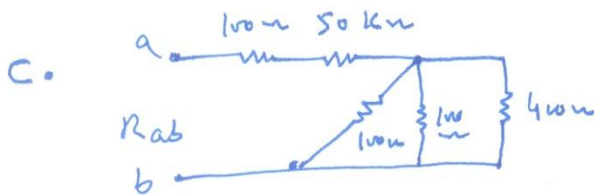b. In ideal voltage source  $R=0$ , with  $R=0$  source transformation is not possible.



$$100 \parallel 100 = \frac{100 \times 100}{200} = 50 \, \Omega$$

$$50 \parallel 400 = \frac{400 \times 50}{450} = 44.45 \, \Omega$$

$$\text{Now } 100 \, \Omega + 50 \, \text{K} \, \Omega + 44.45 \, \Omega =$$

$$144.45 + 50,000 = 50144.45 \, \Omega \approx \boxed{50.1445 \, \text{K} \, \Omega}$$


Question No-2

a. Each e has <sup>charge</sup>  $-1.602 \times 10^{-19} \text{ C}$  so  $4000 \text{ e}$  will have charge

$$-1.602 \times 10^{-19} \times 4000 = \boxed{-6.408 \times 10^{-16} \text{ C}}$$

Each P has charge  $= 1.602 \times 10^{-19} \text{ C}$  so  $80,000,000$  will have charge
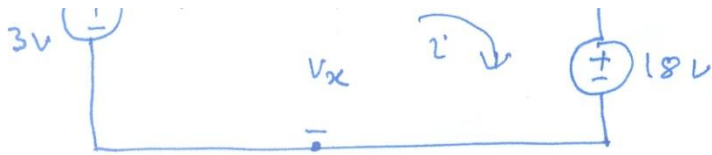
$$1.602 \times 10^{-19} \times 80,000,000 = \boxed{1.2816 \times 10^{-12} \text{ C}}$$



$$\text{KVL on loop} = -3V + 5i + V_x + 18 = 0 \quad \text{--- (1)}$$

KVL on 3V, in  $V_x$

$$= -3 + i + V_x = 0 \quad \text{--- (2)}$$

Subtract (2) from (1)

$$= 4i = -18$$

$$i = -4.5A$$

put up value of  $i$  in eqn 2 or 1

$$-3 + i + V_x = 0$$

$$-3 + (-4.5) + V_x = 0$$

$$-3 - 4.5 + V_x = 0$$

$$V_x = 7.5V$$

$$V_x = 7.5V$$

$$v = 6 \sin 4\pi t \text{ mV} \quad i \text{ at } 0.5s$$

$$i = 6 \sin 4\pi t + 24\pi t \cdot \cos 4\pi t$$

$$6 \sin 4\pi(0.5) + 24\pi(0.5) \cdot \cos 4\pi(0.5)$$

$$6 \sin 2\pi + 12\pi \cdot \cos 2\pi$$

$$0 + 12\pi \cdot \cos 2\pi =$$

$$37.714 \text{ mA} / 37.699 \text{ mA}$$

$$i = \frac{dv}{dt}$$

$$v \frac{dv}{dt} + v \cdot \frac{dv}{dt}$$

$$\sin 4\pi t \cdot 6 + 6t \cdot \cos 4\pi t \cdot 4\pi$$

$$6 \sin 4\pi t + 24\pi t \cdot \cos 4\pi t$$

$$\cos 2\pi = 1$$


$$\sin 2\pi = 0$$

- voltage is the measure of Emf.  $V$  is the pot diff b/w 2x pts.

potmeter is voltage division device, having 3x terminal, variable  $R$ .

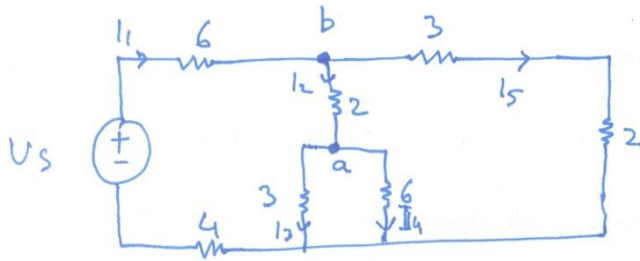rheostat is current controlled device, having 2x terminal,





All R in kΩ

$$I_4 = \frac{1}{2} \text{ mA}$$

Voltage at pt a = 3V ohm law.

i in 3kΩ R = 1A i.e I3

KCL at a = 1 + 0.5 = 1.5 mA thru 2kΩ R i.e I2 = 1.5 mA

V develop at b = (1.5)2 = 3V + 3V (at a) so = 6V

6V dev across 3 & 2kΩ same V in parallel.

i thru 3 & 2kΩ i.e I5 = 6 ÷ 5 = 1.2 mA, ohm law

KCL at b = 1.5 + 1.2 = 2.7 mA i.e I1

V drop at 6kΩ R = 6 × 2.7 = 16.2V


i flows thru 4kΩ R = 2.7 so V dev = (2.7)4 = 10.8V

KVL at left loop =

$$-V_s + 16.2V + 3V + 3V + 10.8V = 0$$

$$V_s = 33V$$

$$33V$$

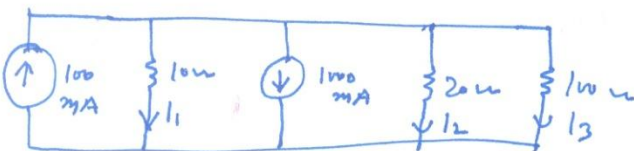


Total i of the set 100mA - 100mA = 900mA in down ward direction

900 i will divide in 3x by 10Ω, 20Ω & 10Ω

$$20 \parallel 10 = \frac{10 \times 20}{10 + 20} = 6.67 \Omega$$
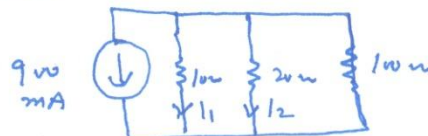
$$I_1 = \left( \frac{6.67}{26.67} \right) 900 = 562.5 \text{ mA}$$




$$10 \parallel 10 = \frac{10 \times 10}{10 + 10} = 5 \Omega$$

$$I_2 = \left( \frac{5}{25} \right) 900 = 281.25 \text{ mA}$$

2.5 C. (1) Electric shock: involuntary contraction of muscles with feeling of pain is electric shock.

MCS-NUST

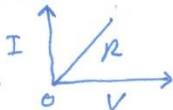(2) Linear Resistance: L.R.s that which obey ohm law i.e.  $V \propto I$  are in proportion while varying, proportionally constant R is a straight line passing through origin or R having constant value of R. R does not change with applied V.



(3) Branch: single element of the circuit having two terminals e.g. V-source or resistance.


(4) Node: where two or more than two element connects or meet or pt connecting 2 or more element. marked with a dot.

(5) Dependent source.

Generate the voltage or current, that is determined by a voltage or current at a specified location in the ckt. Symbol is used to model the electric devices.



d.

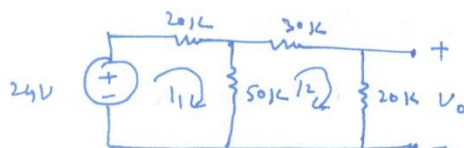

Find  $V_o$

use mesh

mesh 1 KVL:  $-24V + 20I_1 + 50(I_1 - I_2) = 0$   
 $70I_1 - 50I_2 = 24 \rightarrow (1)$

mesh 2 KVL:  $50(I_2 - I_1) + 30I_2 + 20I_2 = 0$   
 $-50I_1 + 100I_2 = 0 \rightarrow (2)$

Solve by 2 substitution =

$I_1 = 2I_2 \rightarrow (3)$

put (3) in (1)

$I_2 = 0.266 \text{ mA}$

$V_o = (20k)(0.266 \text{ mA})$  ohm law

$V_o = \boxed{5.333 \text{ V}}$

Solve two simultaneous eqn.

$I_2 = 0.266 \text{ mA}$

$V_o = (20)(0.266) = 5.333 \text{ V}$